

Experiment No. : 08

Experiment Name: i) Design a synchronous sequential circuit with the sequence given below using JK FFs:

2 → 3 → 4 → 5 → 6 → 1

ii) Design a 4-bit odd counter:


1 → 3 → 5 → 7 → 9 → 11 → 13 → 15

Objective:

The objective of this experiment is to implement two synchronous sequential circuit. In the first experiment we will implement a random synchronous sequential clock counter and in the second experiment we will implement a 4-bit odd counter. In the first experiment we will use 3 JK flip-flops and in the second we will use 4 D flip-flops.

For (i),

State Diagram:

 

State Table:

Present State			Next State		
Q_3	Q_2	Q_1	Q_3	Q_2	Q_1
0	1	0	0	1	1
0	1	1	1	0	0
1	0	0	1	0	1
1	0	1	1	1	0
1	1	0	0	0	1
0	0	1	0	1	0

\therefore There will be 3 JK Flip-Flops

and, $d = \Sigma(0, 7)$

Excitation Table:

Present State			Next State			Flip - Flop					
Q_3	Q_2	Q_1	Q_3	Q_2	Q_1	J_3	K_3	J_2	K_2	J_1	K_1
0	1	0	0	1	1	0	x	x	0	1	x
0	1	1	1	0	0	1	x	x	1	x	1
1	0	0	1	0	1	x	0	0	x	1	x
1	0	1	1	1	0	x	0	1	x	x	1
1	1	0	0	0	1	x	1	x	1	1	x
0	0	1	0	1	0	0	x	1	x	x	1

Function Simplification:

For 3rd Flip-Flop:

For J_3 ,

$Q_3 \backslash Q_2 Q_1$	$Q_2' Q_1'$	$Q_2' Q_1$	$Q_2 Q_1$	$Q_2 Q_1'$
Q_3'	x		1	
Q_3	x	x	x	x

$$\therefore J_3 = Q_2 Q_1$$

For K_3 ,

$Q_3 \backslash Q_2 Q_1$	$Q_2' Q_1'$	$Q_2' Q_1$	$Q_2 Q_1$	$Q_2 Q_1'$
Q_3'	x		x	x
Q_3			x	1

$$\therefore K_3 = Q_2$$

For 2nd Flip-Flop:

For J_2 ,

$Q_3 \backslash Q_2 Q_1$	$Q_2' Q_1'$	$Q_2' Q_1$	$Q_2 Q_1$	$Q_2 Q_1'$
Q_3'	x	1	x	x
Q_3		1	x	

$$\therefore J_2 = Q_1$$

For K_2 ,

$Q_3 \backslash Q_2 Q_1$	$Q_2' Q_1'$	$Q_2' Q_1$	$Q_2 Q_1$	$Q_2 Q_1'$
Q_3'	x	x	1	
Q_3	x	x	x	1

$$\therefore K_2 = Q_3 + Q_1$$

For 1st Flip-Flop:

For J_1 ,

$Q_3 \backslash Q_2 Q_1$	$Q_2' Q_1'$	$Q_2' Q_1$	$Q_2 Q_1$	$Q_2 Q_1'$
Q_3'	x	x	x	1
Q_3	1	x	x	1


$$\therefore J_1 = 1$$

For K_1 ,

$Q_3 \backslash Q_2 Q_1$	$Q_2' Q_1'$	$Q_2' Q_1$	$Q_2 Q_1$	$Q_2 Q_1'$
Q_3'	x	1	1	x
Q_3	x	1	x	x

$$\therefore K_1 = 1$$


Circuit Diagram and IC pin connections:

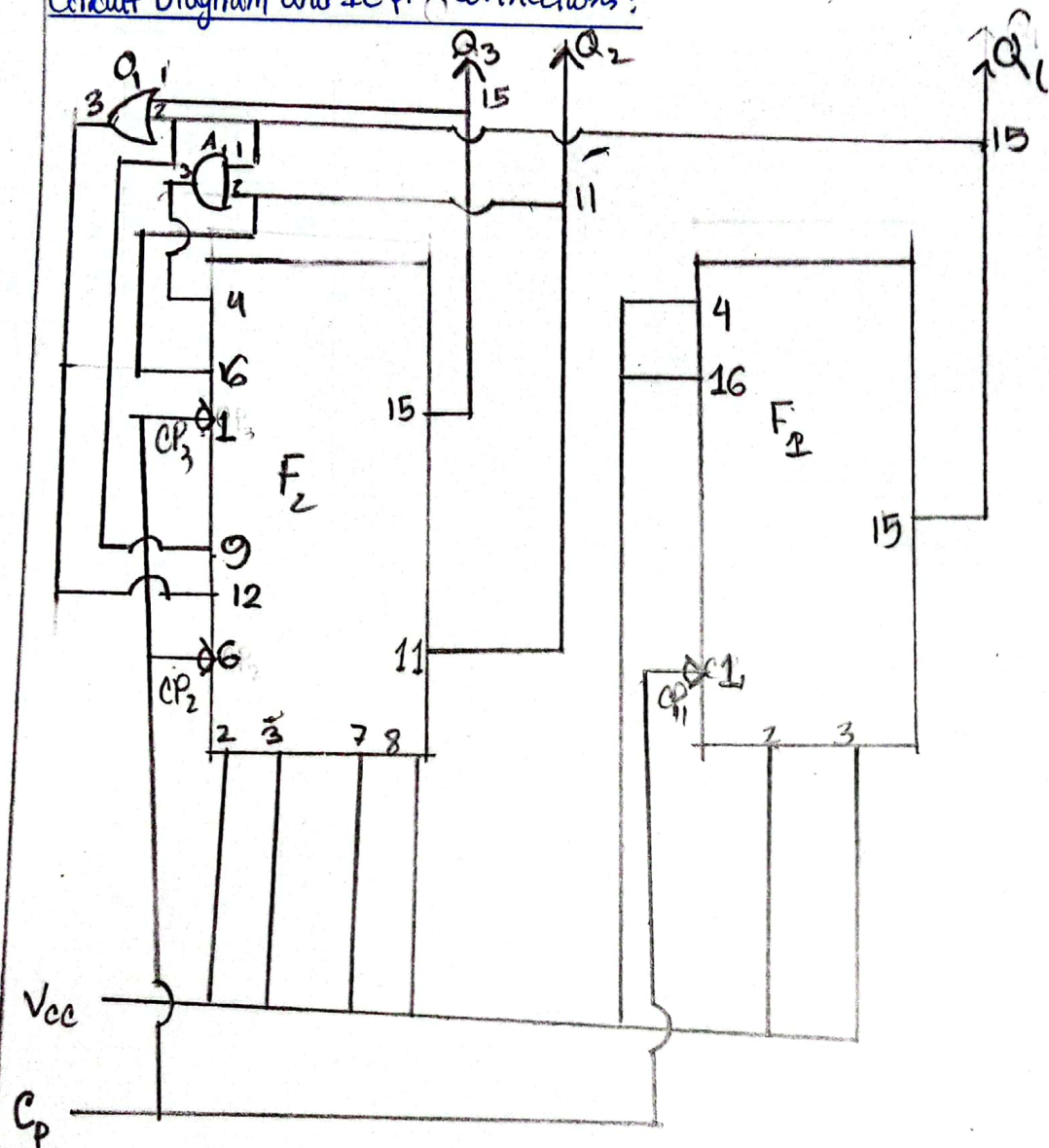

Required ICs:

- i) A₁ — AND Gate (7408); Quantity: 1
- ii) O₁ — OR Gate (7432); Quantity: 1
- iii) F₁, F₂ — JK Flipflop (7476); Quantity: 2

Circuit Diagram and IC pin Connections:

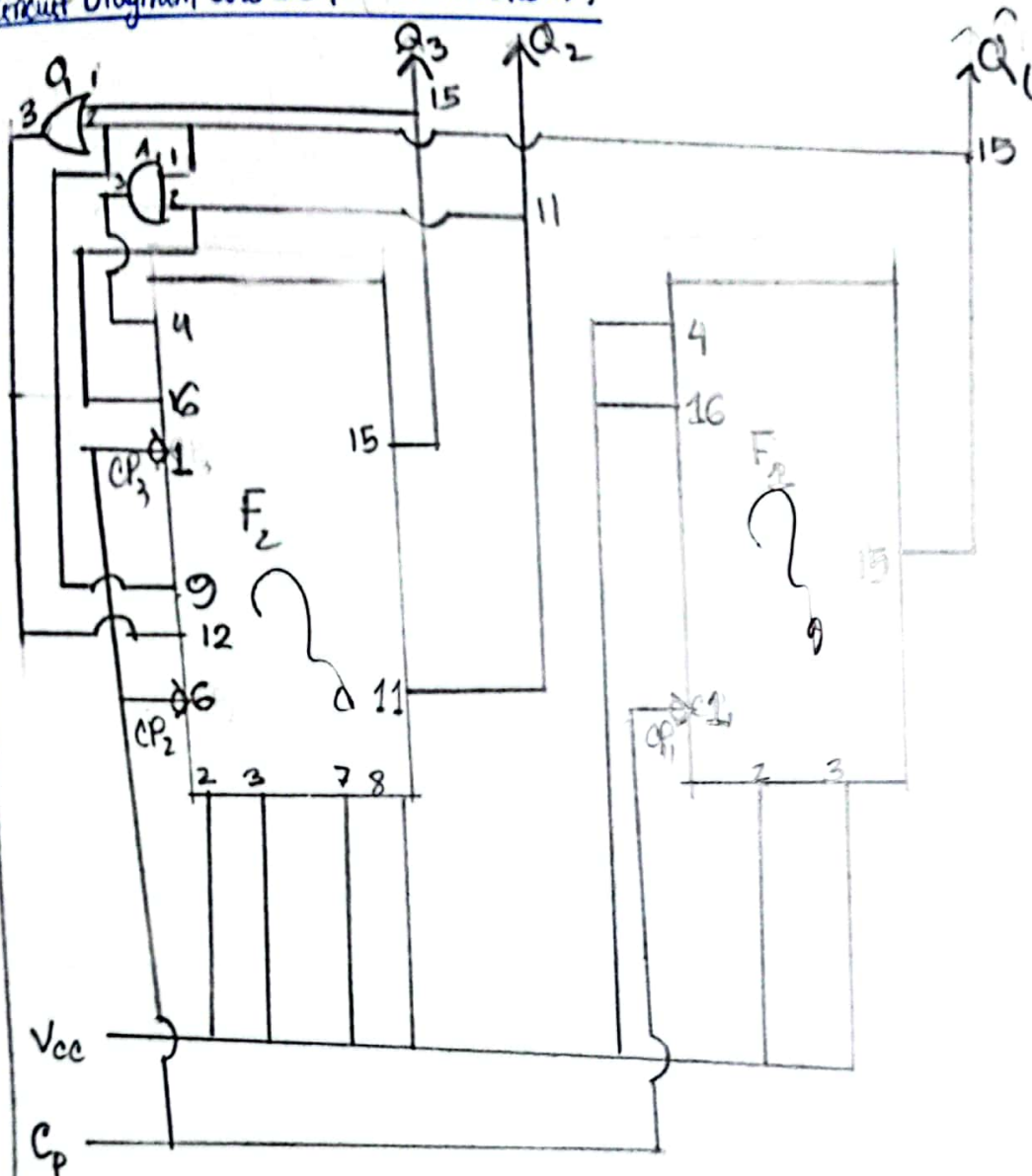


Required ICs:

- i) A_1 — AND Gate (7408); Quantity: 1
- ii) O_1 — OR Gate (7432); Quantity: 1
- iii) F_1, F_2 — JK Flipflop (7476); Quantity: 2

For (ii),

State Diagram:

 

State Table:

Present State				Next State			
Q_4	Q_3	Q_2	Q_1	Q_4	Q_3	Q_2	Q_1
0	0	0	1	0	0	1	1
0	0	1	1	0	1	0	1
0	1	0	1	0	1	1	1
0	1	1	1	1	0	0	1
1	0	0	1	1	0	1	1
1	0	1	1	1	1	0	1
1	1	0	1	1	1	1	1
1	1	1	1	0	0	0	1

\therefore There will be 4 D Flip-Flops

and, $d = \Sigma(0, 2, 4, 6, 8, 10, 12, 14)$

Excitation Table:

Present State				Next State				Flip-Flops			
Q_4	Q_3	Q_2	Q_1	Q_4	Q_3	Q_2	Q_1	D_4	D_3	D_2	D_1
0	0	0	1	0	0	1	1	0	0	1	1
0	0	1	1	0	1	0	1	0	1	0	1
0	1	0	1	0	1	1	1	0	1	1	1
0	1	1	1	1	0	0	1	1	0	0	1
1	0	0	1	1	0	1	1	1	0	1	1
1	0	1	1	1	1	0	1	1	1	0	1
1	1	0	1	1	1	1	1	1	1	1	1
1	1	1	1	0	0	0	1	0	0	0	1

Function Simplification:

For D_4 ,

	Q_4Q_3	Q_2Q_1	$Q_2'Q_1'$	$Q_2'Q_1$	Q_2Q_1	Q_2Q_1'
$Q_4'Q_3'$	X					X
$Q_4'Q_3$	X			1		X
Q_4Q_3	X	1				X
Q_4Q_3'	X	1		1		X

$$\begin{aligned}
 \therefore D_4 &= Q_4Q_3' + Q_4Q_2' + Q_4'Q_3Q_2 \\
 &= Q_4(Q_3' + Q_2') + Q_4'Q_3Q_2; \text{ [Distributive Law]}
 \end{aligned}$$

For D_3 ,

$Q_4 Q_3$	$Q_2 Q_1$	$Q_2' Q_1'$	$Q_2' Q_1$	$Q_2 Q_1'$	$Q_2 Q_1$
$Q_4' Q_3'$	x		1	x	
$Q_4' Q_3$	x	1		x	
$Q_4 Q_3$	x	1		x	
$Q_4 Q_3'$	x		1	x	

$$\therefore D_3 = Q_3 Q_2' + Q_3' Q_2$$

$$= Q_3 \oplus Q_2$$

For D_2 ,

$Q_4 Q_3$	$Q_2 Q_1$	$Q_2' Q_1'$	$Q_2' Q_1$	$Q_2 Q_1'$	$Q_2 Q_1$
$Q_4' Q_3'$	x	1		x	
$Q_4' Q_3$	x	1		x	
$Q_4 Q_3$	x	1		x	
$Q_4 Q_3'$	x	1		x	


$$\therefore D_2 = Q_2'$$

For D_1 ,

$Q_4 Q_3 \backslash Q_2 Q_1$	$Q_2' Q_1'$	$Q_2' Q_1$	$Q_2 Q_1$	$Q_2 Q_1'$
$Q_4' Q_3'$	X	1	1	X
$Q_4' Q_3$	X	1	1	X
$Q_4 Q_3$	X	1	1	X
$Q_4 Q_3'$	X	1	1	X

$$\therefore D_1 = 1$$

Circuit Diagram and IC Pin Connections:

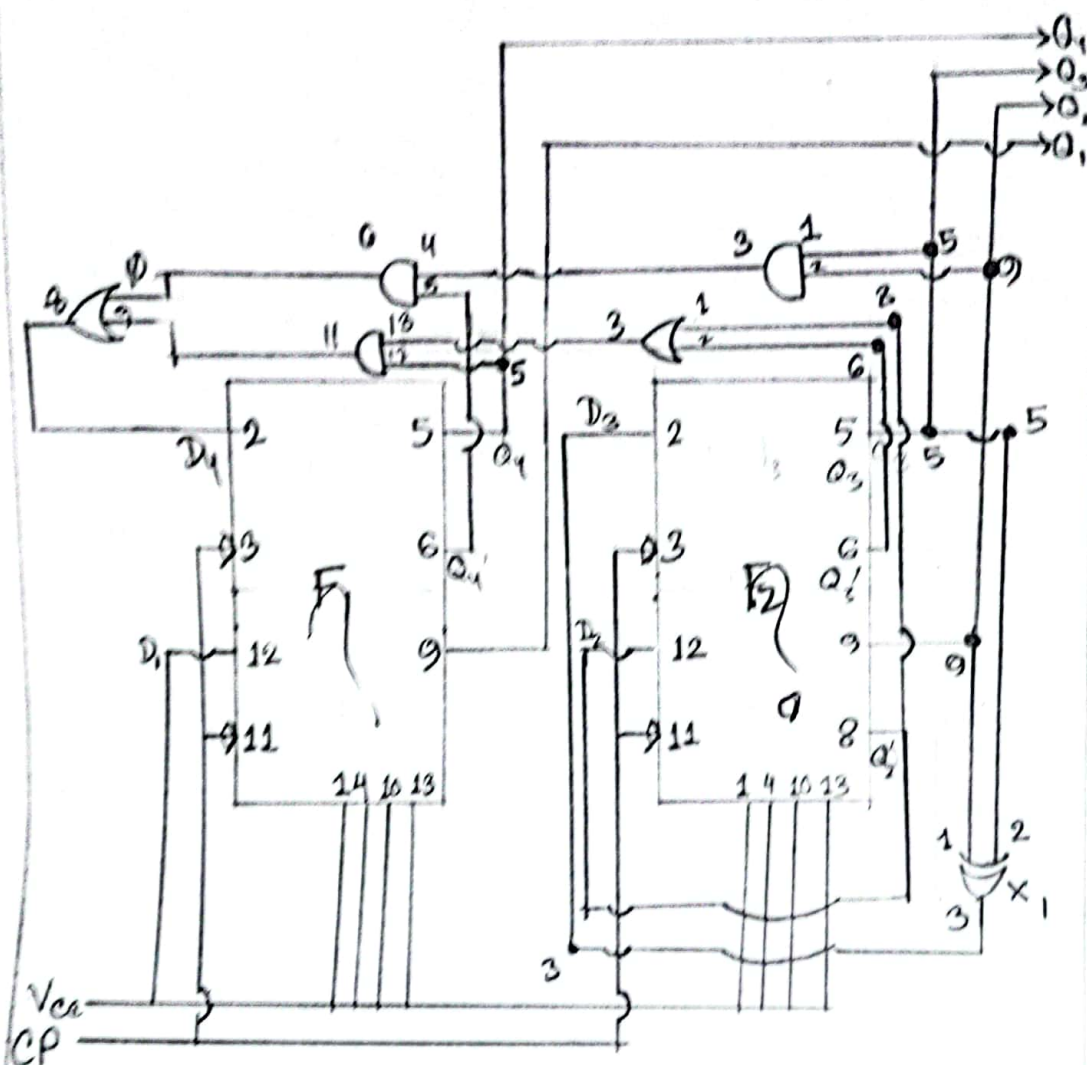

Required ICs:

- i) A_1 — AND Gate (7404); Quantity: 1;
- ii) O_1 — OR Gate (7432); Quantity: 1;
- iii) X_1 — XOR Gate (7486); Quantity: 1;
- iv) F_1, F_2 — D Flip-Flop (7474); Quantity: 2;

Discussion:

Through this experiment, we implemented two synchronous sequential circuits i.e. both circuits had the same clock pass. In the first experiment we implemented a random synchronous sequential clock counter using 3 JK flip-flops and in the second experiment we implemented an 4-bit odd counter using 4 D flip-flops.